

L08: Don't cares

ECE 2195/1170: Algorithms for Complex System Design and Modeling

Dr. Natasa Miskov-Zivanov
Department of Electrical and Computer Engineering
Swanson School of Engineering

Spring 2022




© Natasa Miskov-Zivanov
You may not make copies of this material in any form without my express permission.
Some lecture material and figures courtesy of Rob Rutenbar

1

Don't Cares: 2-level

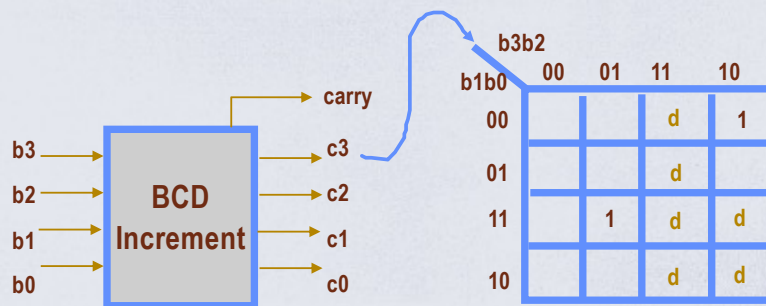- In basic digital design...
 - We told you these were just input patterns that could **never** happen
 - This allowed you to do more simplifications, since you could add a 1 or 0 to the Kmap for that input depending on what was easier to simplify
 - Standard example: BCD incremter circuit



Patterns $b_3 b_2 b_1 b_0 = 1010, 1011, 1100, 1101, 1110, 1111$ cannot happen

3

Don't Cares: Multi-level


- To say this differently
 - In basic 2-level designs somebody told you what inputs wouldn't happen...
 - *...and you just believed them!*
- What's different in multi-level?
 - Can still have these sorts of don't cares at the primary inputs of the Boolean logic network....
 - ...but there can also be don't cares **arising from structure** of the network
 - These latter kind are very useful for simplifying the individual vertices in the Boolean logic network
 - *But, you have to go find these don't cares explicitly*



4

Informal Tour of DCs in Multilevel Networks

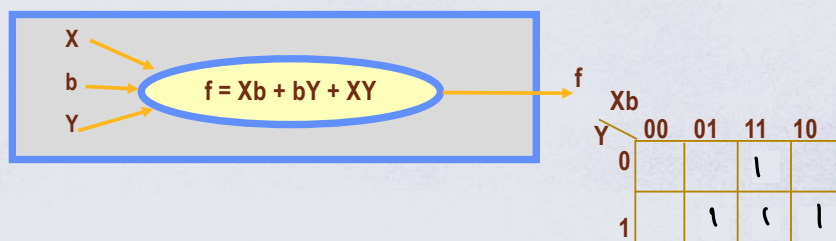- Suppose we have a Boolean network...
 - And we are looking at node “f” in that network
- Can we say anything about don't cares for node f?
 - **NO**
 - We don't know any “context” for surrounding parts of network
 - As far as we can tell, all patterns of inputs **(X,b,Y)** are possible




5

Informal Multilevel DC Tour

- OK, suppose we know this about input X to f
 - Node X is actually $a \cdot b$
 - Now can we say something about **DCs** for node f ...?
 - **YES**

B is input to both x and f

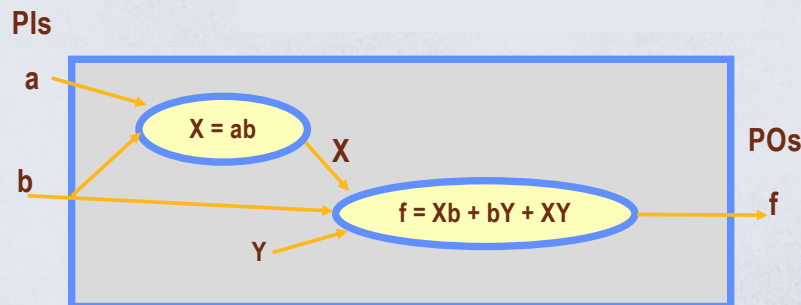


6

Are there any impossible patterns for X , b , and Y ? \rightarrow Use DCs

Informal Multilevel DC Tour

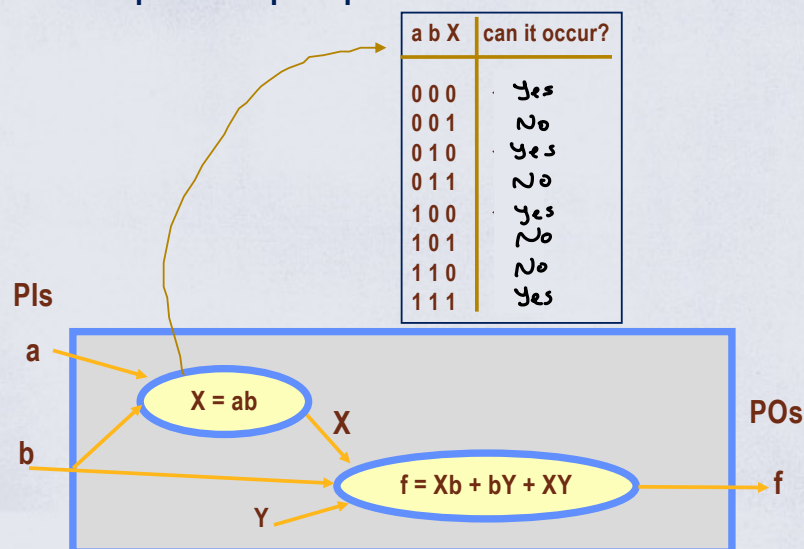
- Go list all the input/output patterns for node X



7

Informal Multilevel DC Tour

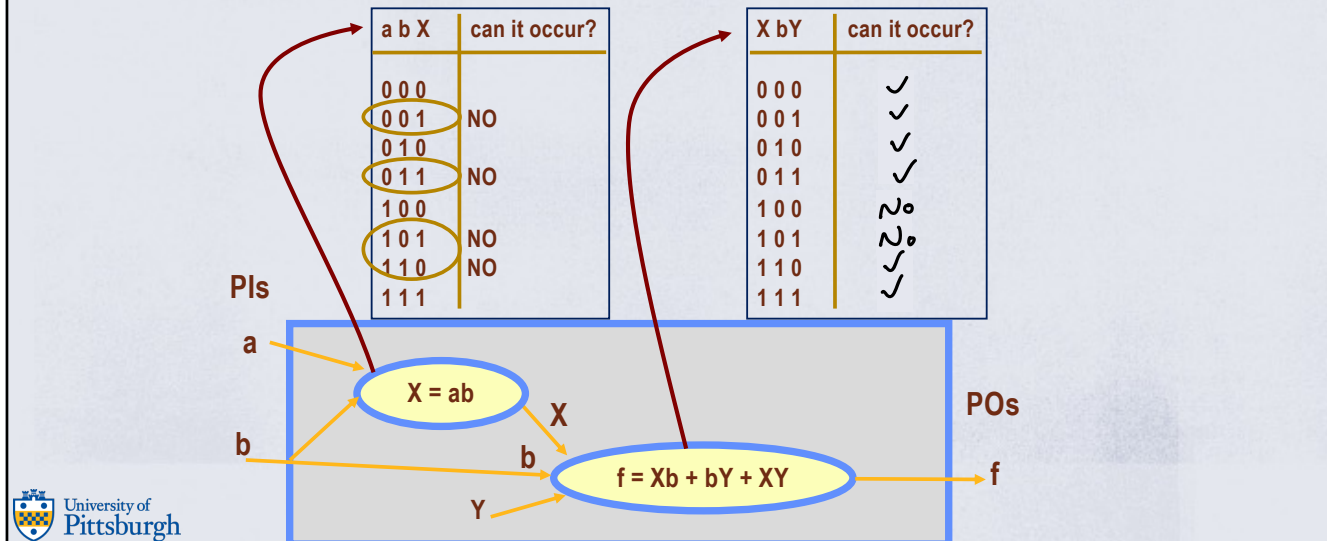
- Impossible $a b X$ patterns \rightarrow impossible $X b Y$ patterns?



8

Informal Multilevel DC Tour

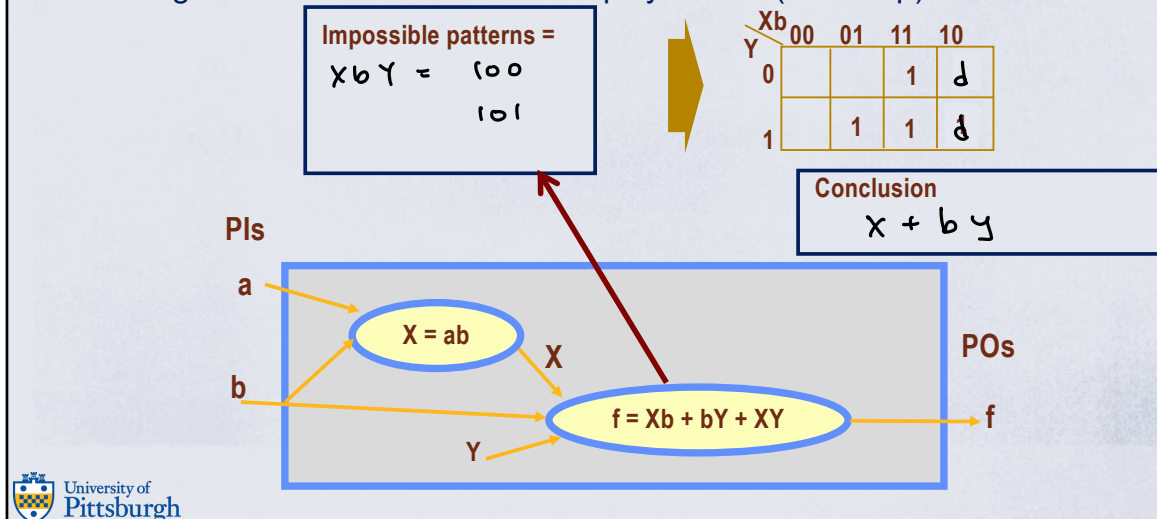
- Impossible $X b Y$ patterns give us DCs for node f
 - Change how we would want to simplify node f (its Kmap)



9

Informal Multilevel DC Tour

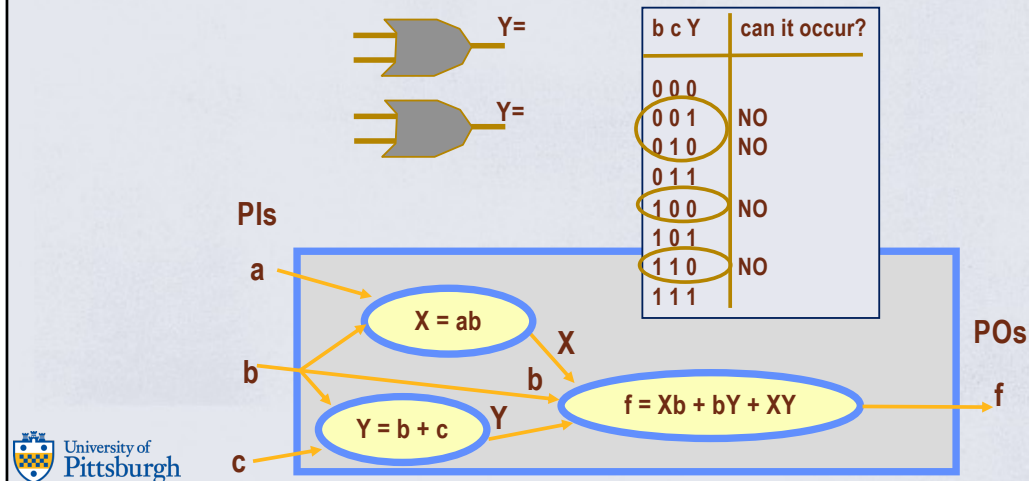- OK, what if we now know $Y = b+c$ as well?
 - Can do this again at Y ...are there impossible patterns of $b\ c\ Y$?




10

Informal Multilevel DC Tour

- OK, can we (again) get impossible patterns on $X\ b\ Y$?

$$y = b + c$$


$$x = ab$$

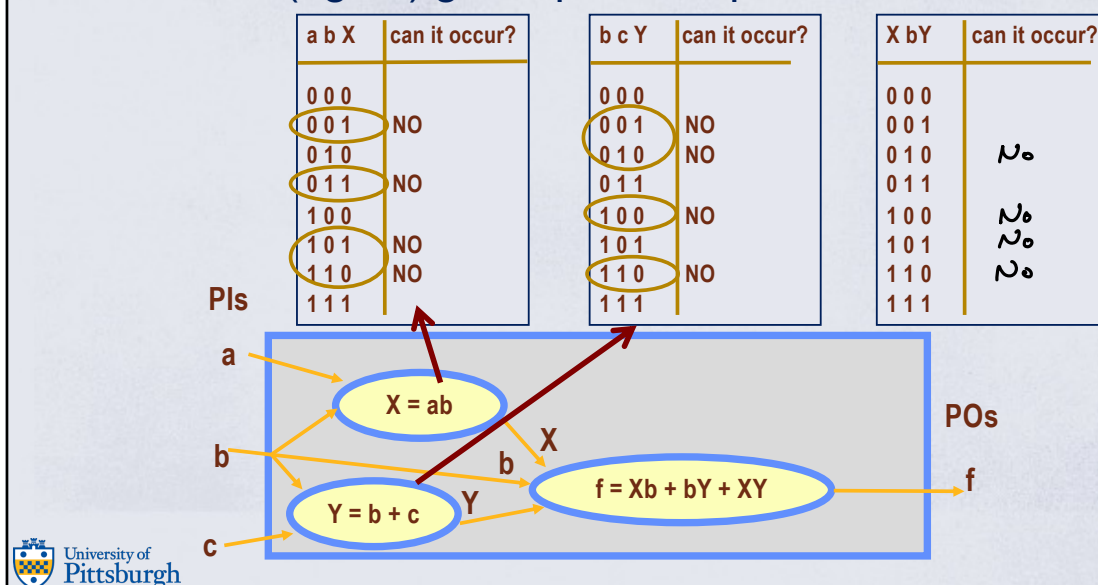

11

Informal Multilevel DC Tour

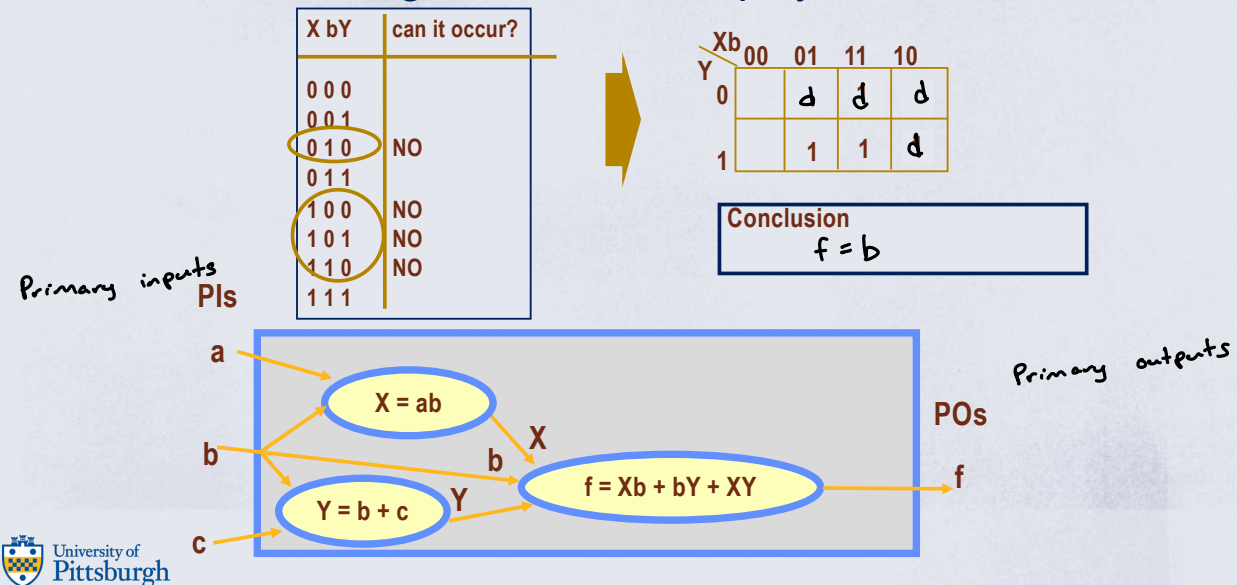
- OK, do these change how we'd simplify inside f ?



12

Informal Multilevel DC Tour

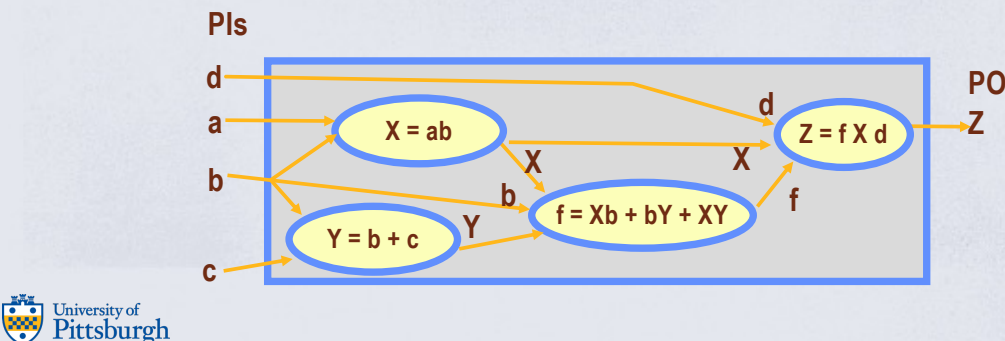- OK, now suppose f is *not* a primary output, Z is...
 - **Question:** when does a change in the output of node f actually **propagate** through to change the primary output Z , i.e., the output of the overall Boolean logic network
 - Or, reverse question: when does it **not matter** what f is...?
 - Let's go look at patterns of $f X d$ at node Z ...



13


Informal Multilevel DC Tour

f	X	d	Z does it change?
0	0	0	No, $z = 0$
1	0	0	
0	0	1	No, $z = 0$
1	0	1	
0	1	0	No, $z = 0$
1	1	0	
0	1	1	Yes, $z = f$
1	1	1	

Patterns at input to f node itself that are DCs just because those patterns make Z output *insensitive* to changes in f

$$X b Y$$

$$= 0 \text{ --}$$

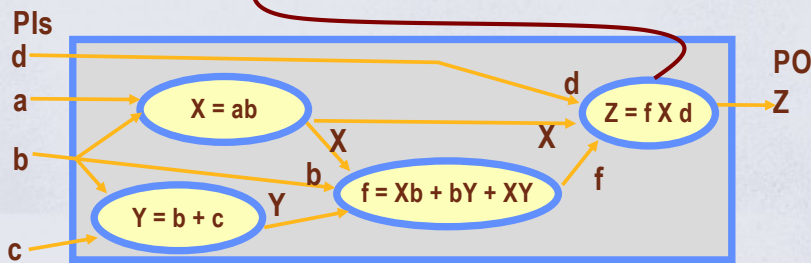

Informal Multilevel DC Tour


- OK, can we use this $X=0$ DC pattern to simplify f more?

Patterns at input to f node itself that are DCs just because those patterns make Z output *insensitive* to changes in f

$$\Rightarrow X b Y = 0 \text{ --}$$


Xb	00	01	11	10
Y				
0	d	d	d	d
1	d	d	1	d

Conclusion
 $f = 1$

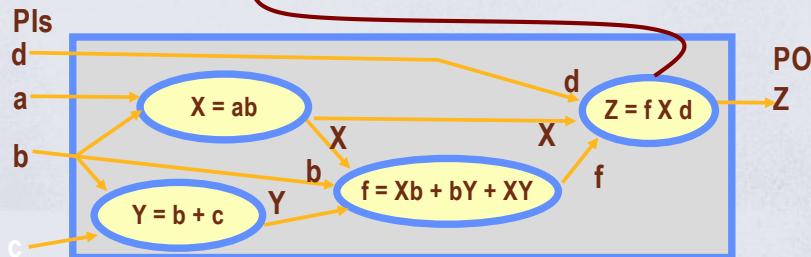


Informal Multilevel DC Tour

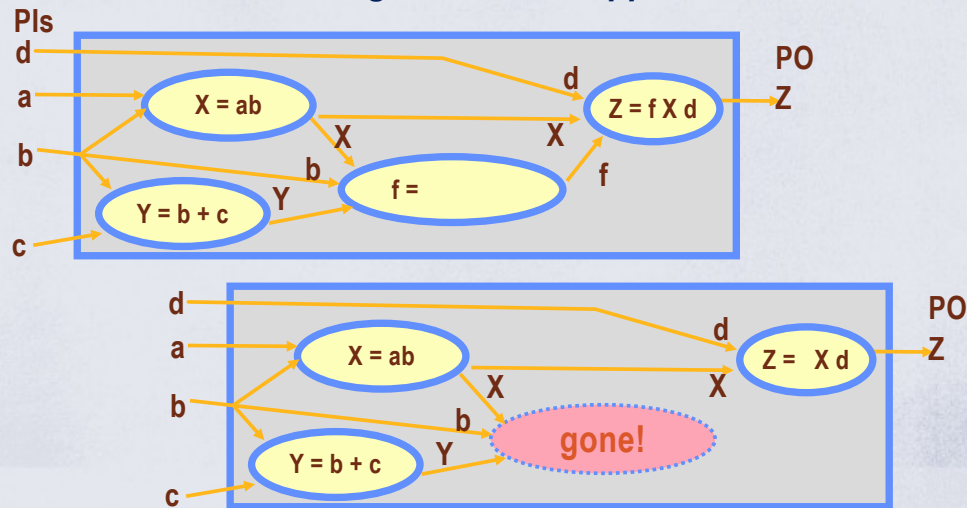- Hey, look what happened to f node...
 - *Due to context of surrounding nodes, it disappeared!*



Informal Multilevel DC Tour

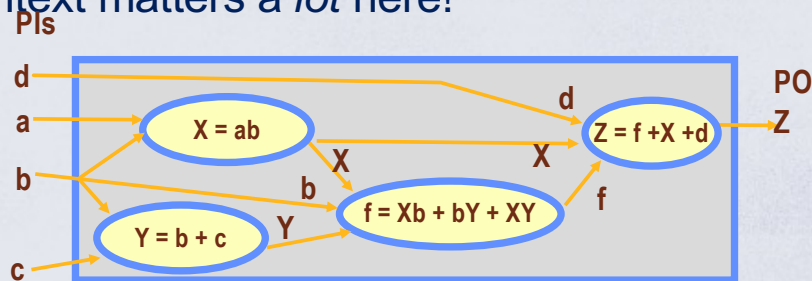- OK, suppose instead that PO $Z = f + X + d$ (OR not AND)
 - What changes?
 - **Answer:** patterns at f inputs that make Z insensitive to changes in f
 - There are still impossible patterns of $(f X d)$ but you cannot specify any of them exactly only knowing the $(X b Y)$ inputs to f
 - f doesn't disappear, it simplifies to $f = b$ (*go check...*)
- Network context matters a *lot* here!



Formal View of These DCs

- Overall, there are 3 types of formal DCs...
 - **Satisfiability** don't cares
 - Patterns that can't occur on (inputs, output) of one network node...
 - ... because of internal structure of multi-level logic
 - **Controllability** don't cares
 - Global, external: patterns that can't happen at primary inputs to our overall Boolean network (these are the DCs you already knew about)
 - Local, internal: patterns that can't happen at inputs to a network vertex
 - **Observability** don't cares
 - Patterns at input of a vertex that prevent outputs of the network from being sensitive to changes in output of that vertex
 - Patterns that "mask" outputs
- Next lecture: See if we can clarify where these each come from...



18

ECE 2195/1170: Next lecture

- More on DCs



ECE 2195/1170, Spring 2022

19

19