

Homework Assignment #5

ECE 0257 – Spring 2019

Name

Avery Peiffer

Collaborators

Daniel Stumpp

Book Problems

Sedra & Smith 5.17

Sedra & Smith 5.18

Sedra & Smith 5.20

Sedra & Smith 5.41

Sedra & Smith 5.44

Sedra & Smith 5.50

Sedra & Smith 5.54

Sedra & Smith 5.55 (part a only)

Simulation Problems

Exercises (a) – (d)

Check-list Before Submission

- ☐ Write within boxes, no boxes are moved
- ☐ Write your full names in designated area
- ☐ Save this file as a PDF before uploading, keep the number of pages (**16**) unchanged
- ☐ Notify “TO BE CONTINUED” accordingly if you used the extra pages (page 14-16)

Sedra & Smith 5.17

5.17

$V_t = 0.8 \text{ V}$ V_{DS} small
 $V_{GS} = 1.2 \text{ V}$, $r_{DS} = 1 \text{ k}\Omega$
 $V_{OV} = 0.4 \text{ V}$

$r_{DS} = \frac{1}{k_n(V_{GS} - V_t)}$

$1000 = \frac{1}{k_n' \frac{W}{L} (0.4)}$

$\frac{W}{L} = \frac{1}{400 k_n'}$

$200 = \frac{1}{k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)}$

$200 = \frac{1}{k_n' \left(\frac{1}{400 k_n'}\right) (V_{GS} - 0.8)}$

$V_{GS} = 2.8 \text{ V}$

$\left(\frac{W}{L}\right)' = 2 \left(\frac{W}{L}\right)$

$r = \frac{1}{\frac{2}{400} (2)} = 100 \Omega$

5.18

$V_t = 0.5 \text{ V}$

Saturation Region

$\rightarrow V_{GS}$ and min. V_{DS}

Avery Pei
 CoE 025
 Homework

Sedra & Smith 5.18

$V_{DS} = 0.4 \text{ V}$
 $r_{DS} = \frac{1}{k_n (V_{GS} - V_t)}$
 $1000 = \frac{1}{1 \cdot \frac{W}{L} (0.4)}$
 $\frac{W}{L} = \frac{1}{400 k_n}$
 $\left(\frac{W}{L}\right)' = 2 \left(\frac{W}{L}\right)$
 $r = \frac{1}{\frac{2}{400} (2)} = 100 \Omega$

$200 = \frac{1}{k_n' \left(\frac{1}{400 k_n}\right) (V_{GS} - 0.8)}$
 $V_{GS} = 2.8 \text{ V}$

5.18
 $V_{th} = 0.5 \text{ V}$
 $k_n' \left(\frac{W}{L}\right) = 1.6 \frac{\text{mA}}{\text{V}^2}$
 Saturation Region
 $i_D = 50 \mu\text{A}, i_D = 200 \mu\text{A} \rightarrow V_{GS} \text{ and min. } V_{DS}$

$50 \times 10^{-6} \text{ A} = \frac{1}{2} \left(1.6 \frac{\text{mA}}{\text{V}^2}\right) \left(\frac{1 \text{ A}}{1000 \text{ mA}}\right) (V_{GS} - 0.5)^2 \Rightarrow V_{GS} = 0.75 \text{ V}$
 $V_{DS, \min} = 0.25 \text{ V}$

$200 \times 10^{-6} \text{ A} = \frac{1}{2} \left(1.6 \frac{\text{mA}}{\text{V}^2}\right) \left(\frac{1 \text{ A}}{1000 \text{ mA}}\right) (V_{GS} - 0.5)^2 \Rightarrow V_{GS} = 1 \text{ V}$
 $V_{DS, \min} = 0.5 \text{ V}$

5.20
 $k_n' = 400 \frac{\text{mA}}{\text{V}^2}$
 $V_t = 0.5 \text{ V}$
 In saturation region:
 $2 \times 10^{-3} \text{ A} = \frac{1}{2} \left(400 \frac{\text{mA}}{\text{V}^2}\right) \left(\frac{1 \text{ A}}{10^6 \mu\text{A}}\right) \left(\frac{W}{0.18 \times 10^{-6} \text{ m}}\right) (V_{GS} - 0.5)^2$

Sedra & Smith 5.20

5.18

$$V_{th} = 0.5 \text{ V}$$

$$k'_n \left(\frac{W}{L} \right) = 1.6 \frac{\text{mA}}{\text{V}^2}$$

Saturation Region

$$i_D = 50 \mu\text{A}, i_D = 200 \mu\text{A} \rightarrow V_{GS} \text{ and min. } V_{DS}$$

$$50 \times 10^{-6} \text{ A} = \frac{1}{2} \left(1.6 \frac{\text{mA}}{\text{V}^2} \right) \left(\frac{1 \text{ A}}{1000 \text{ mA}} \right) (V_{GS} - 0.5)^2 \Rightarrow V_{GS} = 0.75 \text{ V}$$

$$V_{DS, \min} = 0.25 \text{ V}$$

$$200 \times 10^{-6} \text{ A} = \frac{1}{2} \left(1.6 \frac{\text{mA}}{\text{V}^2} \right) \left(\frac{1 \text{ A}}{1000 \text{ mA}} \right) (V_{GS} - 0.5)^2 \Rightarrow V_{GS} = 1 \text{ V}$$

$$V_{DS, \min} = 0.5 \text{ V}$$

5.20

$$k'_n = 400 \frac{\text{mA}}{\text{V}^2}$$

$$V_{th} = 0.5 \text{ V}$$

$$V_{GS} = V_{DS} = V_{supply} = 1.8 \text{ V}$$


$$I_D = 2 \text{ mA} \quad L = 0.18 \mu\text{m}$$

In saturation region:

$$2 \times 10^{-3} \text{ A} = \frac{1}{2} \left(400 \frac{\text{mA}}{\text{V}^2} \right) \left(\frac{1 \text{ A}}{10^6 \mu\text{A}} \right) \left(\frac{W}{0.18 \times 10^{-6} \text{ m}} \right) (1.8 - 0.5)^2$$

$$W = 1.07 \mu\text{m}$$

5.41

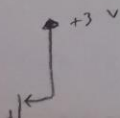

$$V_{th} = -0.5 \text{ V}$$

$$V_G: +3 \text{ V} \rightarrow 0 \text{ V},$$

all three modes

$$2.5 < V_G \leq 3: \text{ Cutoff Region}$$

$$0.5 < V_G \leq 2.5: \text{ Linear Region}$$

1.5: Saturation Region

Sedra & Smith 5.41

$$200 \times 10^{-6} \text{ A} = \frac{1}{2} \left(1.6 \frac{\text{mA}}{\text{V}^2} \right) \left(\frac{1 \text{ A}}{1000 \text{ mA}} \right) (V_{GS} - 0.5)^2 \Rightarrow \boxed{V_{GS} = 1 \text{ V}}$$

$$\boxed{V_{DS, \min} = 0.5 \text{ V}}$$

5.20

$$K_n' = 400 \frac{\text{mA}}{\text{V}^2}$$

$$V_t = 0.5 \text{ V}$$

$$V_{GS} = V_{DS} = V_{\text{supply}} = 1.8 \text{ V}$$

$$I_D = 2 \text{ mA} \quad L = 0.18 \text{ mm}$$


In saturation region:

$$2 \times 10^{-3} \text{ A} = \frac{1}{2} \left(400 \frac{\text{mA}}{\text{V}^2} \right) \left(\frac{1 \text{ A}}{10^6 \text{ mA}} \right) \left(\frac{W}{0.18 \times 10^{-6} \text{ m}} \right)^2$$

$$(1.8 - 0.5)^2$$

$$\boxed{W = 1.07 \text{ mm}}$$

5.41

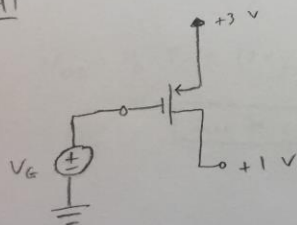

$V_{tp} = -0.5 \text{ V}$
 $V_E: +3 \text{ V} \rightarrow 0 \text{ V}$,
 all three modes


$2.5 \leq V_G \leq 3$: Cutoff Region

$0.5 \leq V_G \leq 2.5$: Linear Region

$0 \leq V_G \leq 0.5$: Saturation Region

Sedra & Smith 5.44

5.44

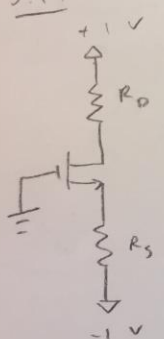

Establish:

- $I_D = 0.1 \text{ mA}$
- $V_{DS} = +0.3 \text{ V}$
- $V_t = 0.5 \text{ V}$
- $\mu_n C_{ox} = 400 \frac{\mu\text{A}}{\text{V}^2} = 4 \times 10^{-4} \frac{\text{A}}{\text{V}^2}$
- $L = 0.4 \mu\text{m}$
- $W = 5 \mu\text{m}$

???

$V_{ov} = V_{GS} - V_t$

Saturation Region: $V_{DS} \geq V_{ov}$

$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{+1 \text{ V} - 0.3 \text{ V}}{0.1 \text{ mA}} = 7 \text{ k}\Omega$

$R_S = \frac{-0.7 - (-1)}{0.1 \times 10^{-3} \text{ A}} = 3 \text{ k}\Omega$

$V_{DS} > V_{ov}$: Saturation Region


$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = \frac{1}{2} (4 \times 10^{-4} \frac{\text{A}}{\text{V}^2}) (\frac{5}{0.4}) V_{ov}^2 = 0.1 \times 10^{-3} \text{ A}$

$V_{ov} = 0.2 \text{ V}$ $V_{GS} = V_t + V_{ov} = 0.7 \text{ V}$

50 +2.5 V

Sedra & Smith 5.50

$V_{DS} \approx V_G$: Saturation region
 $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = \frac{1}{2} (4 \times 10^{-4} \frac{A}{V^2}) (\frac{5}{0.4}) V_{ov}^2 = 0.1 \times 10^{-3} A$
 $V_{ov} = 0.2 V \quad V_{GS} = V_G + V_{ov} = 0.7 V$

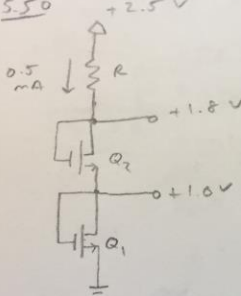5.50


NMOS:
 $V_G = 0.5 V$
 $\mu_n C_{ox} = 250 \frac{\mu A}{V^2} = 250 \times 10^{-6} \frac{A}{V^2}$
 $\lambda = 0$
 $L_1 = L_2 = 0.25 \mu m$
 Find W_{Q1} , W_{Q2} , R to
 obtain indicated voltage,
 current values

$R = \frac{2.5 V - 1.8 V}{0.5 mA} = \boxed{1.4 k\Omega}$

Q_2 : $V_{DS} = 1.8 V - 1.0 V = 0.8 V$
 $V_{GS} = 1.8 V - 1.0 V = 0.8 V$ } Saturation
 $0.5 \times 10^{-3} A = \frac{1}{2} (250 \times 10^{-6} \frac{A}{V^2}) (\frac{W}{0.25 \mu m}) (0.8 V - 0.5 V)^2$


$\boxed{W_2 = 11.1 \mu m}$

Q_1 : Also saturation
 $0.5 \times 10^{-3} A = \frac{1}{2} (250 \times 10^{-6} \frac{A}{V^2}) (\frac{W}{0.25 \mu m}) (1.0 V - 0.5 V)^2$

$\boxed{W_1 = 4 \mu m}$

Sedra & Smith 5.54

5.54

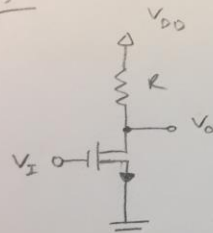

$V_t = 0.4 \text{ V}$
 $k_n' = 500 \times 10^{-6} \frac{\text{A}}{\text{V}^2}$
 $\lambda = 0$
 $V_I = V_{DD} = +1.3 \text{ V} \rightarrow r_{DS} = 50 \text{ } \Omega, V_O = 50 \text{ mV}$
 Find $\frac{W}{L}$ and R
 $V_{DS} = 50 \text{ mV} \rightarrow \text{LINEAR region}$

$$50 \text{ } \Omega = k_n' \frac{W}{L} \left(V_{OV} - \frac{1}{2} V_{DS} \right)$$

$$V_{OV} = V_I - V_t = 0.9 \text{ V}$$

$$\frac{1}{50} \text{ } \Omega = \left(500 \times 10^{-6} \frac{\text{A}}{\text{V}^2} \right) \frac{W}{L} (0.9 \text{ V} - 0.025 \text{ V})$$

$$\frac{W}{L} = 45.71$$

$$\frac{V_{DD} - V_O}{R} = I_D \rightarrow \frac{(1.3 \text{ V} - 0.05 \text{ V})}{R} = \left(500 \times 10^{-6} \frac{\text{A}}{\text{V}^2} \right) (45.71) (0.9 - 0.025)$$

$$R = 1.25 \text{ k}\Omega$$

Let $L = 10 \text{ } \mu\text{m}$
 Then $W = 457.1 \text{ } \mu\text{m}$

$I_D = 4 \text{ mA} = 4 \times 10^{-3} \text{ A}$ $\lambda = 0$

Sedra & Smith 5.55 (part a only)

5.55 $|V_t| = 1 \text{ V}$, $k'_n \frac{W}{L} = 4 \frac{\text{mA}}{\text{V}^2}$, $\lambda = 0$

(a) Assume Saturation:

$$I_D = \frac{1}{2} k_n V_{ov}^2 \quad V_{GS} = |V_t| + V_{ov} = 1 + 1 = 2 \text{ V}$$

$$2 = \frac{1}{2} (4) V_{ov}^2 \quad V_1 = 0 - V_{GS} = -2 \text{ V}$$

$$V_{ov} = 1 \text{ V} \quad V_2 = 5 - 2(2) = 1 \text{ V}$$

$V_{DS} = +1 \text{ V} \rightarrow$ Saturation is correct

(b) Assume Saturation:

$$I_D = \frac{1}{2} k_n V_{ov}^2 \quad V_{GS} = |V_t| + V_{ov} = 1 + 1 = 2 \text{ V}$$

$$2 = \frac{1}{2} (4) V_{ov}^2 \quad V_3 = 2 \text{ V}$$

$$V_{ov} = 1 \text{ V}$$

\rightarrow Saturation is correct

(c) Assume Saturation:

$$I_D = \frac{1}{2} k_n V_{ov}^2 \quad V_{SG} = |V_t| + V_{ov} = 2 \text{ V} = V_4$$

$$2 = \frac{1}{2} (4) V_{ov}^2 \quad \frac{V_{DG} - 5}{1.5 \text{ k}\Omega} = 2 \quad V_{DG} = -2 \text{ V} = V_5$$

$$V_{ov} = 1 \text{ V}$$

\rightarrow Saturation is correct

(d) Assume Saturation:

$$I_D = \frac{1}{2} k_n V_{ov}^2 \quad V_{SG} = 1 + 1 = 2 \text{ V}$$

$$2 = \frac{1}{2} (4) V_{ov}^2 \quad V_5 - V_6 = 2$$

$$V_{ov} = 1 \text{ V} \quad 5 - V_6 = 2$$


$$V_6 = 3 \text{ V}$$

$$V_6 - V_7 = 2$$

$$3 - V_7 = 2$$


$$V_7 = 1 \text{ V}$$

Simulation Exercise (a)

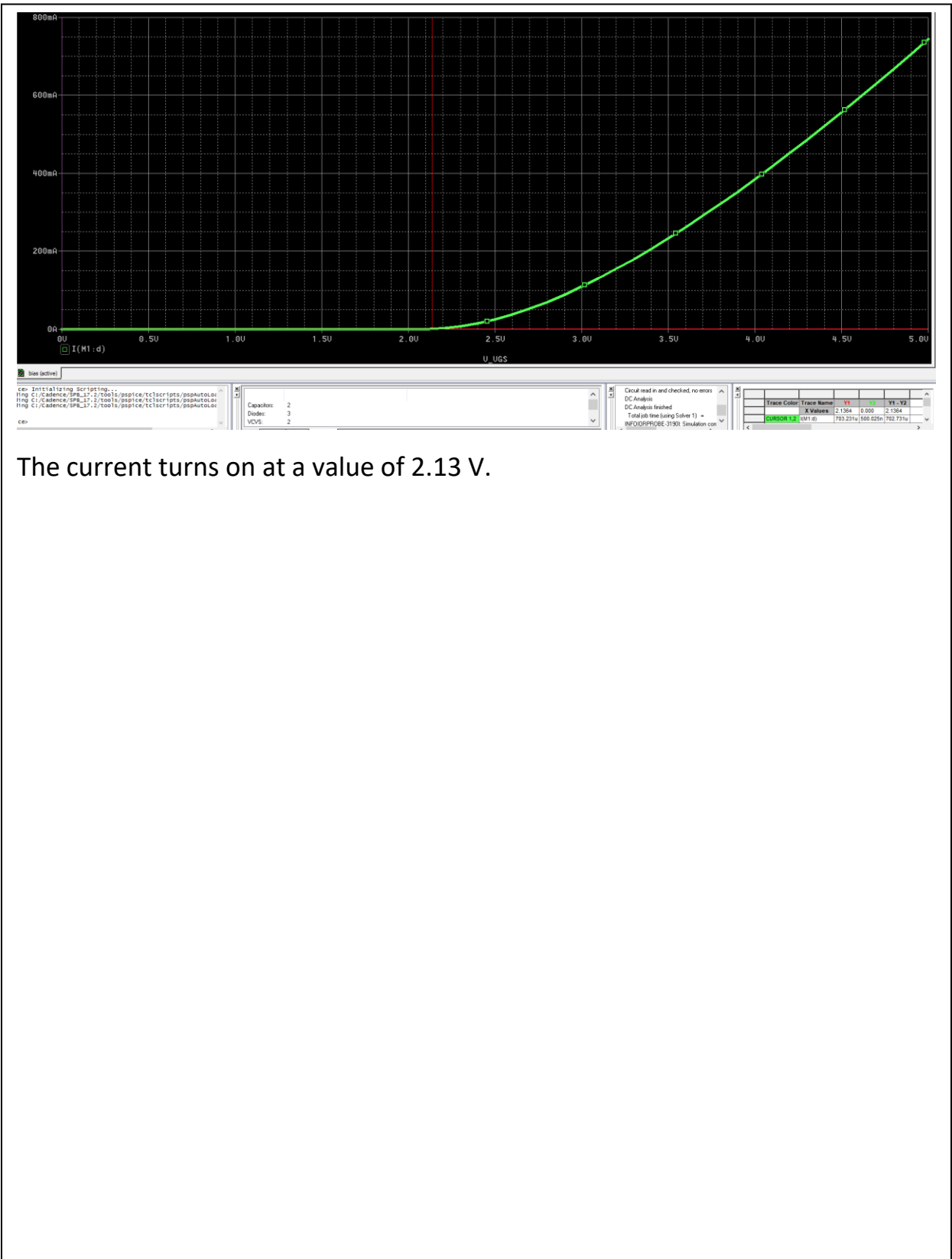


The current turns on at a value of 2.13 V.

Simulation Exercise (b)

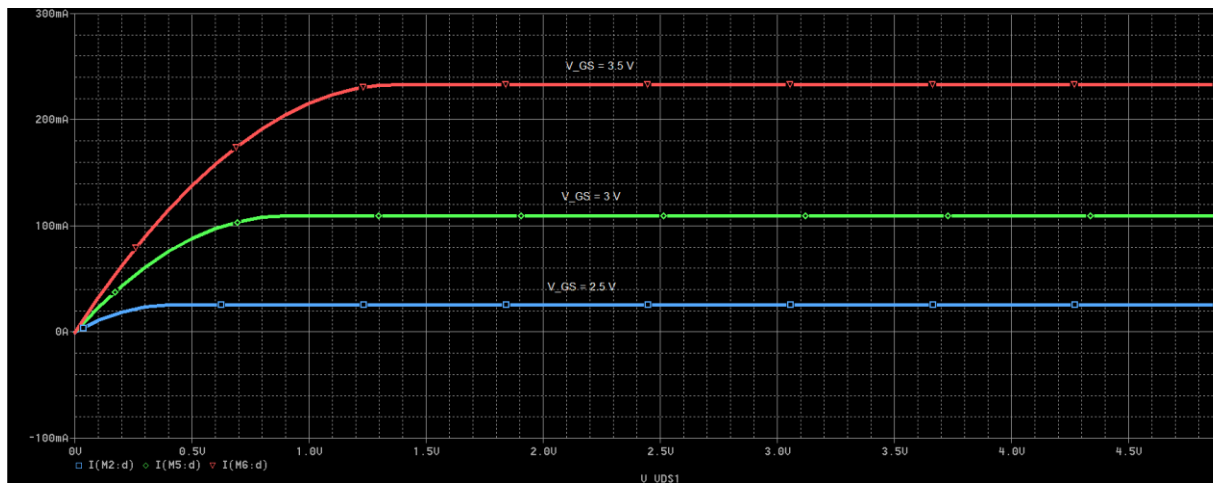


In case it is tough to see, the bottom line is $V_{GS} = 2.5 \text{ V}$ (blue), the middle is $V_{GS} = 3 \text{ V}$ (green), and the top line is $V_{GS} = 3.5 \text{ V}$ (red).

Simulation Exercise (c)

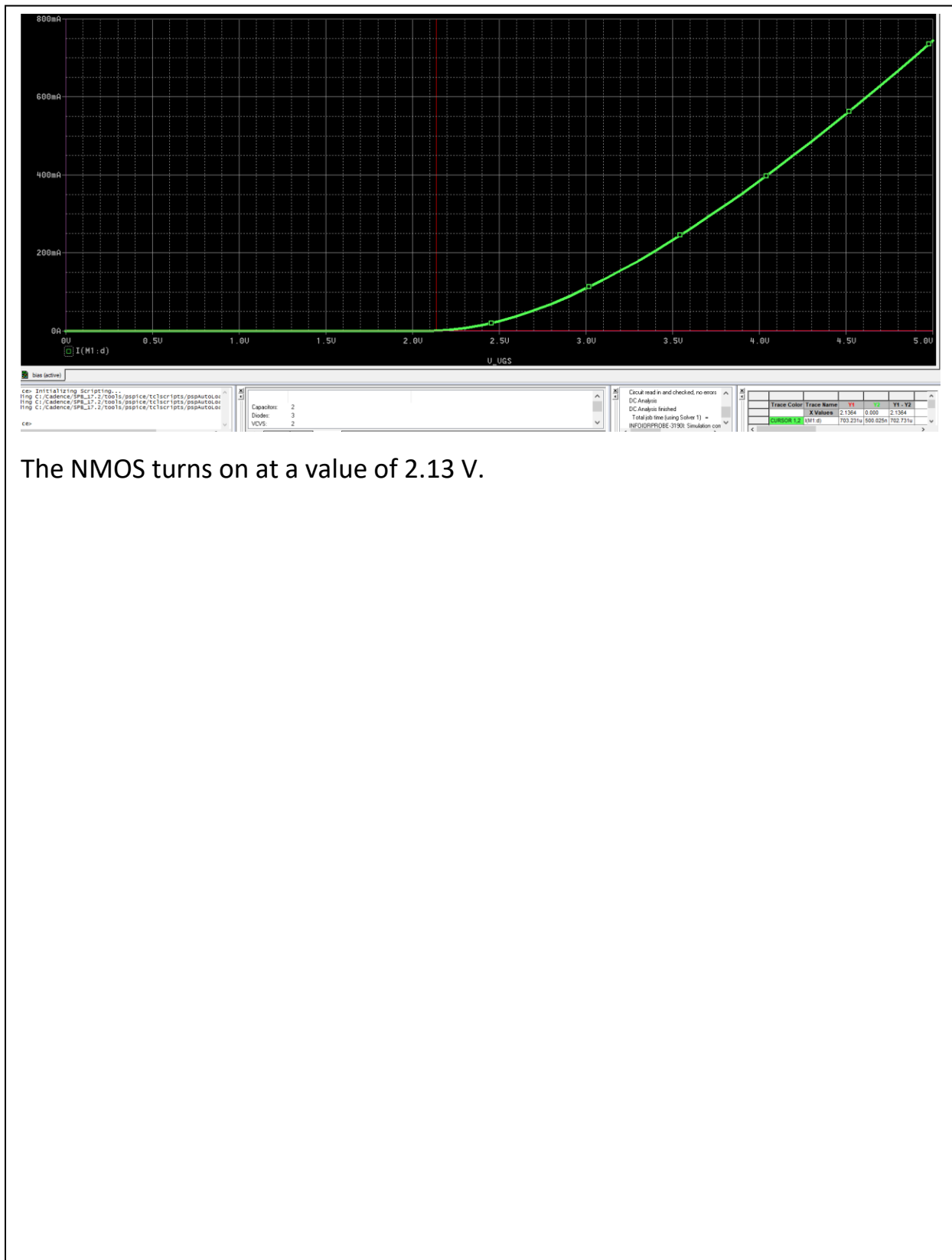

The NMOS turns on at a value of 2.13 V.

Simulation Exercise (d)

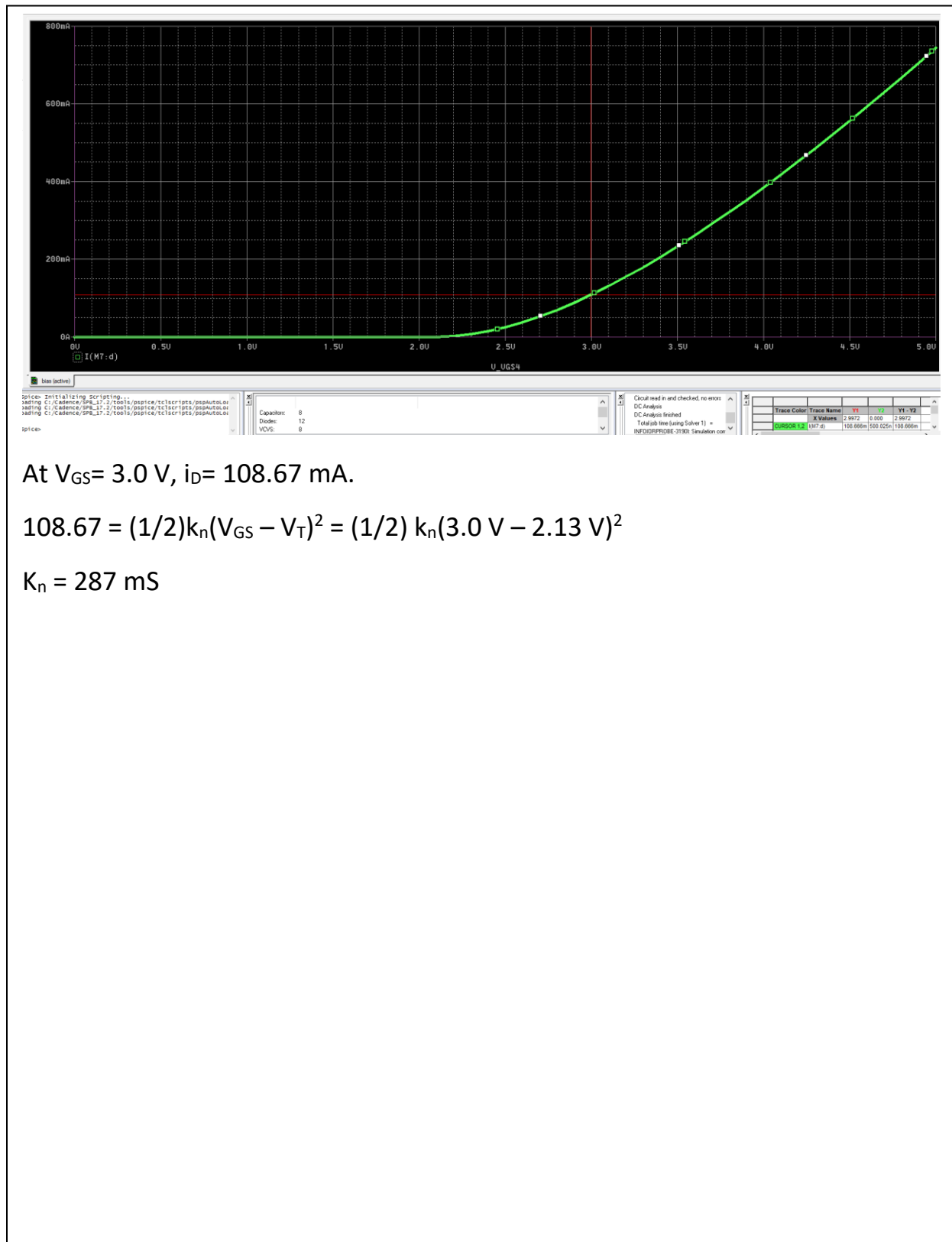

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]