

Homework Assignment #4

ECE 0257 – Spring 2019

Full Name

Avery Peiffer

Collaborators

Daniel Stumpp

Book Problems

Sedra & Smith 4.80
Sedra & Smith 5.4
Sedra & Smith 5.9
Sedra & Smith 5.10
Sedra & Smith 5.12
Sedra & Smith 5.14

Simulation Problems

DC power supply design

Check-list Before Submission

- ☐ Write within boxes, no boxes are moved
- ☐ Write your full names in designated area
- ☐ Save this file as a PDF before uploading, keep the number of pages (**16**) unchanged
- ☐ Notify “TO BE CONTINUED” accordingly if you used the extra pages (page 14-16)

Sedra & Smith 4.80

Avery Peiffer
CoE 0257
Homework 4

4.80
DC output voltage of 12 V
 ± 1 V ripple
Load = 200 Ω
Line voltage = 120 V rms
60 Hz
Diodes have 0.7 V drop

(a) rms voltage = $\frac{12.7 + 1 \text{ V ripple}}{\sqrt{2}} = 9.69 \text{ V}$

(b) Ripple = 2 V
 $V_R = V_{PR} \frac{T}{RC} \Rightarrow 2 = 13 \frac{1}{60(200)C} \Rightarrow C = 542 \text{ } \mu\text{F}$

(c) $V_S = -V_P = 13.7 \text{ V} = \text{Peak Reverse Voltage}$
PIV = 1.5 (Max Reverse) = 20.55 V

(d) $i_{D, \text{avg}} = I_L (1 + \pi \sqrt{\frac{V_P}{V_R}}) = 721 \text{ mA}$
 $V_{o, \text{avg}} = \frac{-1}{2\pi} \int_0^{3.086} (12.7 \sin \phi - 0.7) d\phi = -3.699 \text{ V}$
 $I_{o, \text{avg}} = 18.5 \text{ mA}$


(e) Peak current = $\frac{12.7 - 0.7}{200 \Omega} = 60 \text{ mA}$

5.4
(a) $2V_{ov} = 2(V_{GS} - V_T)$
 $1/2$

(b) $2W \rightarrow 1/2$

$R_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)}$

Sedra & Smith 5.4

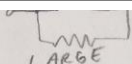

 LARGE

(a) rms voltage = $\frac{12.7 + 1 \text{ V ripple}}{\sqrt{2}} = \boxed{9.69 \text{ V}}$

(b) Ripple = 2 V

$V_R = V_{PFC} \frac{T}{60(200) \text{ s}} \Rightarrow \boxed{C = 542 \text{ mF}}$

(c) $V_S = -V_P = \boxed{13.7 \text{ V}}$ = Peak Reverse Voltage

PIV = 1.5 (Max Reverse) = $\boxed{20.55 \text{ V}}$

(d) $I_{D, \text{avg}} = I_L (1 + \pi \sqrt{\frac{2V_P}{V_A}}) = \boxed{721 \text{ mA}}$

$V_{o, \text{avg}} = \frac{1}{2\pi} \int_{0.05515}^{3.086} (12.7 \sin \phi - 0.7) d\phi = -3.699 \text{ V}$

$I_{o, \text{avg}} = 18.5 \text{ mA}$

(e) Peak current = $\frac{12.7 - 0}{200} = \boxed{60 \text{ mA}}$

5.4

(a) $2V_{ov} = 2(V_{GS} - V_T)$

$R_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)}$

(b) $2W \rightarrow 1/2$

(c) Unchanged $\rightarrow 1$

(d) Thickness halved - C_{ox} doubled $\rightarrow W$ and L cancel each other

$1/2$

5.9

$k_n = 4 \frac{\text{mA}}{\text{V}^2}$ $V_t = 0.5 \text{ V}$ $V_{GS} = 1.0 \text{ V}$

Saturation Region: $V_{DS} \geq V_{ov}$

$V_{DS} = \boxed{0.5 \text{ V}}$

Sedra & Smith 5.9

5.4

(a) $2V_{ov} = 2(V_{GS} - V_T)$
 $\frac{1}{2}$

$$R_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)}$$

$I_{D,avg} = 18.5 \text{ mA}$

(e) Peak current = $\frac{12.7 - 0}{200}$

$= 60 \text{ mA}$

(b) $2W \rightarrow \frac{1}{2}$

(c) Unchanged $\rightarrow 1$

(d) Thickness halved - C_{ox} doubled $\rightarrow W$ and L cancel each other
 $\frac{1}{2}$

5.9

$k_n = 4 \frac{\text{mA}}{\text{V}^2}$ $V_t = 0.5 \text{ V}$ $V_{GS} = 1.0 \text{ V}$

Saturation Region: $V_{DS} \geq V_{ov}$

$V_{DS} \geq (1.0 \text{ V} - 0.5 \text{ V}) = 0.5 \text{ V}$

$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{ov}^2$

$= \frac{1}{2} k_n V_{ov}^2 = \frac{1}{2} \left(4 \frac{\text{mA}}{\text{V}^2} \right) (0.5 \text{ V})^2 = 0.5 \text{ mA}$

Sedra & Smith 5.10

5.10

$$L_{min} = 0.25 \mu m$$

$$t_{ox} = 6 nm$$

$$\mu_n = 450 \frac{cm^2}{V \cdot s}$$

$$V_t = 0.5 V$$

$$(a) C_{ox} = \frac{3.9 \epsilon_0}{t_{ox}} = \frac{3.9 (8.85 \times 10^{-12} \frac{F}{m})}{6 \times 10^{-9} m} = .0057525 \frac{F}{m^2}$$

$$K'_n = \mu_n C_{ox} = (.045 \frac{m^2}{V \cdot s}) (.0057525 \frac{F}{m^2}) = 2.59 \times 10^{-4} \frac{F}{V \cdot s}$$

$$\mu_n = 450 \frac{cm^2}{V \cdot s} = .045 \frac{m^2}{V \cdot s}$$

$$(b) \frac{W}{L} = \frac{20 \mu m}{0.25 \mu m}$$

$$I_D = 0.5 mA$$

$$V_{ov}$$

$$V_{GS}$$

$$V_{DSmin}$$

$$\text{Saturation Region: } 0.5 mA = \frac{1}{2} (2.59 \times 10^{-4} \frac{F}{V \cdot s}) (\frac{20}{0.25}) V_{ov}^2$$

$$V_{ov} = 0.2197 V$$

$$V_{GS} = V_{ov} + V_t = 0.7197 V$$

$$V_{DSmin} = V_{ov} = 0.2197 V$$

(c) Operate as 100Ω resistor for very small V_{DS}
 V_{ov}, V_{GS}

$$\frac{I}{100 \Omega} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)$$

$$\frac{I}{100 \Omega} = (2.59 \times 10^{-4} \frac{F}{V \cdot s}) (\frac{20}{0.25}) (V_{GS} - 0.5 V)$$

$$V_{GS} = 0.983 V$$

$$V_{ov} = 0.483 V$$

5.12

$$\mu_p = 0.4 \mu_n$$

Equal channel lengths

Equal drain currents and overdrive voltages

Equal drain currents and overdrive voltages

Sedra & Smith 5.12

(b) $\frac{W}{L} = \frac{20 \mu\text{m}}{0.25 \mu\text{m}}$ V_{ov} V_{GS} $V_{DS \min}$ $I_D = 0.5 \text{ mA}$

Saturation Region: $0.5 \text{ mA} = \frac{1}{2} (2.59 \times 10^{-4} \frac{\text{F}}{\text{V}^2}) (\frac{20}{0.25}) V_{ov}^2$

$$V_{ov} = 0.2197 \text{ V}$$

$$V_{GS} = V_{ov} + V_T = 0.7197 \text{ V}$$

$$V_{DS \min} = V_{ov} = 0.2197 \text{ V}$$

(c) Operate as 100Ω resistor for very small V_{DS}
 V_{ov}, V_{GS}

$$\frac{I}{100 \Omega} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

$$\frac{I}{100 \Omega} = (2.59 \times 10^{-4} \frac{\text{F}}{\text{V}^2}) (\frac{20}{0.25}) (V_{GS} - 0.5 \text{ V})$$

$$V_{GS} = 0.983 \text{ V}$$

$$V_{ov} = 0.483 \text{ V}$$

5.12

$$\mu_p = 0.4 \mu\text{m}$$

Equal channel lengths

Equal drain currents and overdrive voltages

Relative widths ($\frac{W_p}{W_n}$)

$$\frac{I}{0.4} = 2.5 \text{ times wider}$$

Sedra & Smith 5.14

5.14

$$t_{ox} = 6 \text{ nm}$$

$$\mu_n = 460 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} = .046 \frac{\text{m}^2}{\text{V}\cdot\text{s}}$$

$$V_t = 0.5 \text{ V}$$

$$\frac{W}{L} = 10$$

Find I_D

$$(a) V_{GS} = 2.5 \text{ V and } V_{DS} = 1 \text{ V}$$

Triode Region:

$$I_D = K_n' \left(\frac{W}{L} \right) \left(V_{GS} - \frac{1}{2} V_{DS} - V_t \right) V_{DS}$$

$$C_{ox} = \frac{3.9 \epsilon_0}{t_{ox}} = \frac{3.9 (8.85 \times 10^{-12})}{6 \times 10^{-9}} = .0057525$$

$$I_D = (.046 \frac{\text{m}^2}{\text{V}\cdot\text{s}}) (.0057525) (10) \left(2 - \frac{1}{2} \right) (1)$$

$$I_D = 3.9 \text{ mA}$$

$$(b) V_{GS} = 2 \text{ V and } V_{DS} = 1.5 \text{ V}$$

Saturation Region

$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L} \right) V_{OV}^2 = \frac{1}{2} (.046 \frac{\text{m}^2}{\text{V}\cdot\text{s}}) (.0057525) (10) (2 - 0.5)^2$$

$$1 \quad K_n' = \mu_n C_{ox} \quad I_D = 2.98 \text{ mA}$$

$$(c) V_{GS} = 2.5 \text{ V and } V_{DS} = 0.2 \text{ V}$$

Linear Region

$$I_D = (.046 \frac{\text{m}^2}{\text{V}\cdot\text{s}}) (.0057525) (10) (2.5 - 0.5) 0.2 = 1.06 \text{ mA}$$

$$(d) V_{GS} = V_{DS} = 2.5 \text{ V}$$

$$I_D = \frac{1}{2} (.046 \frac{\text{m}^2}{\text{V}\cdot\text{s}}) (.0057525) (10) (2.5 \text{ V} - 0.5 \text{ V})^2 = 5.29 \text{ mA}$$

$L_1 = 2 \text{ H}$
 $L_2 = 27.2 \text{ mH}$

Calculations: $N_1/N_2 = V_1/V_2$

$N_1/N_2 = 120 \text{ V}/14 \text{ V}$

$N_1/N_2 = 60 \text{ winds}/7 \text{ winds}$

$N_1/N_2 = \sqrt{L_1/L_2} \quad 60/7 = \sqrt{L_1/L_2}$

$L_1/L_2 = 73.469$, Let $L_1 = 2 \text{ H}$ then $L_2 = 27.2 \text{ mH}$


The graph displays two voltage signals over time. The x-axis represents time from 0s to 100ms, and the y-axis represents voltage from -200V to 200V. The red signal, $U(R1:1)$, is a high-frequency oscillation with a period of approximately 10ms. The green signal, $U(T1:3)$, is a lower-frequency oscillation with a period of approximately 20ms. Both signals are plotted with markers at each data point.

VOFF = 0
/AMPL = 169.7056275
FREQ = 60
AC =


AC LINE 0V 0A 1 0V 0A TX1 7.655e-24A 7.655e-21V XFMR_OUT

0 0V 0A -7.655e-24A 7.655e-21V R2 100M 7.655e-24A

DC power supply design 2(a)

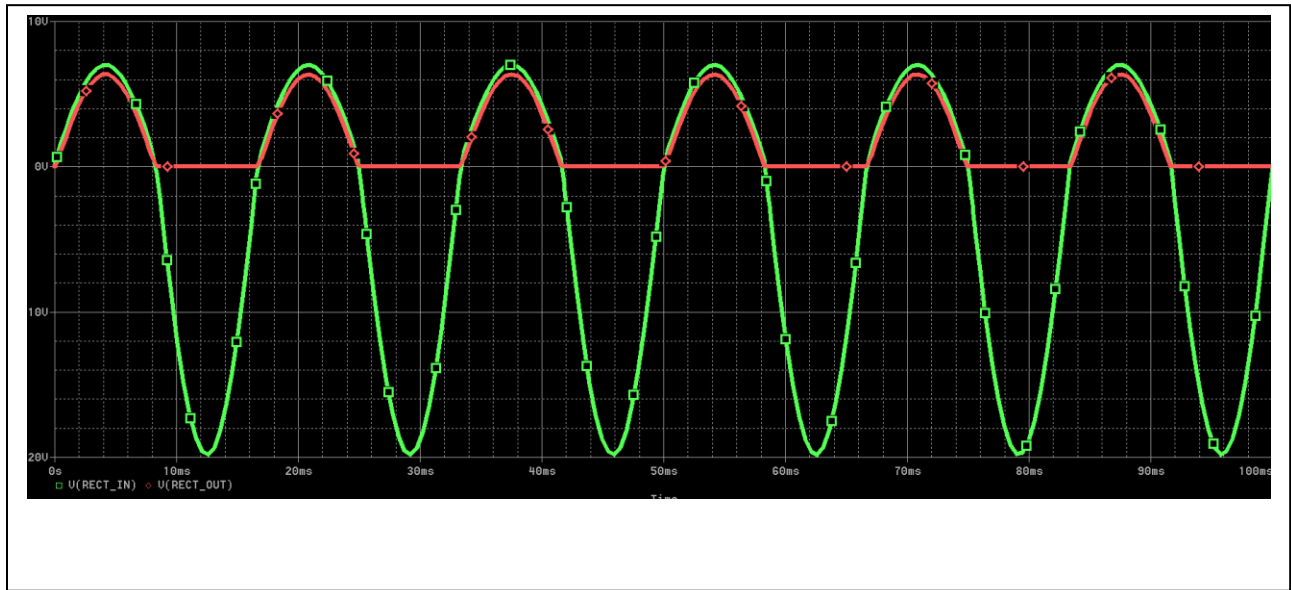

DC power supply design 2(b)

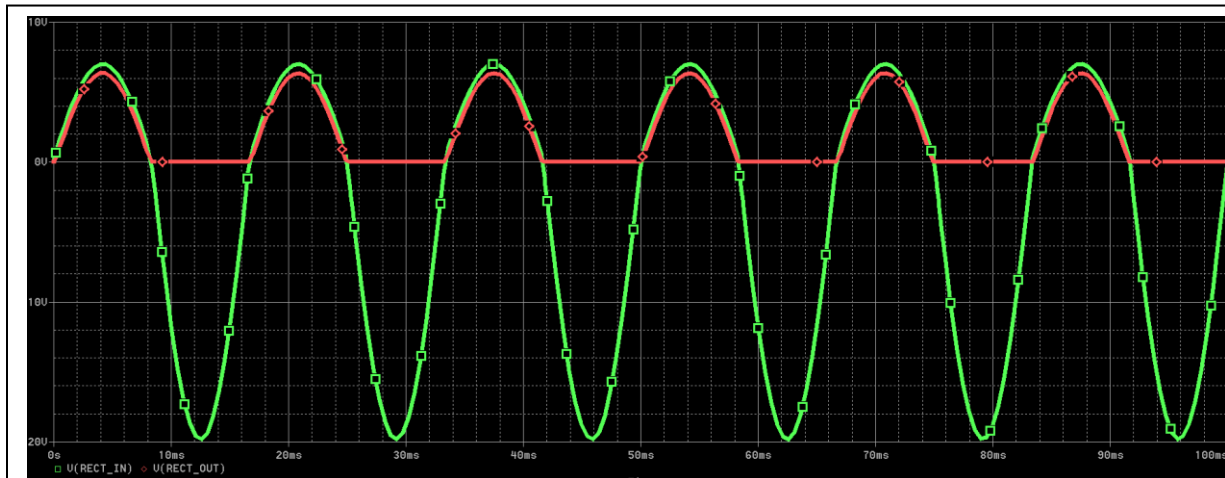

Cursor Calculations: Left Click on V(RECT_IN) at peak, Right Click on V(RECT_OUT) immediately below

V(RECT_IN) = 7.0032 V


V(RECT_OUT) = 6.3538 V

$V_d = .6494 \text{ V}$

DC power supply design 3(a)



DC power supply design 3(b)

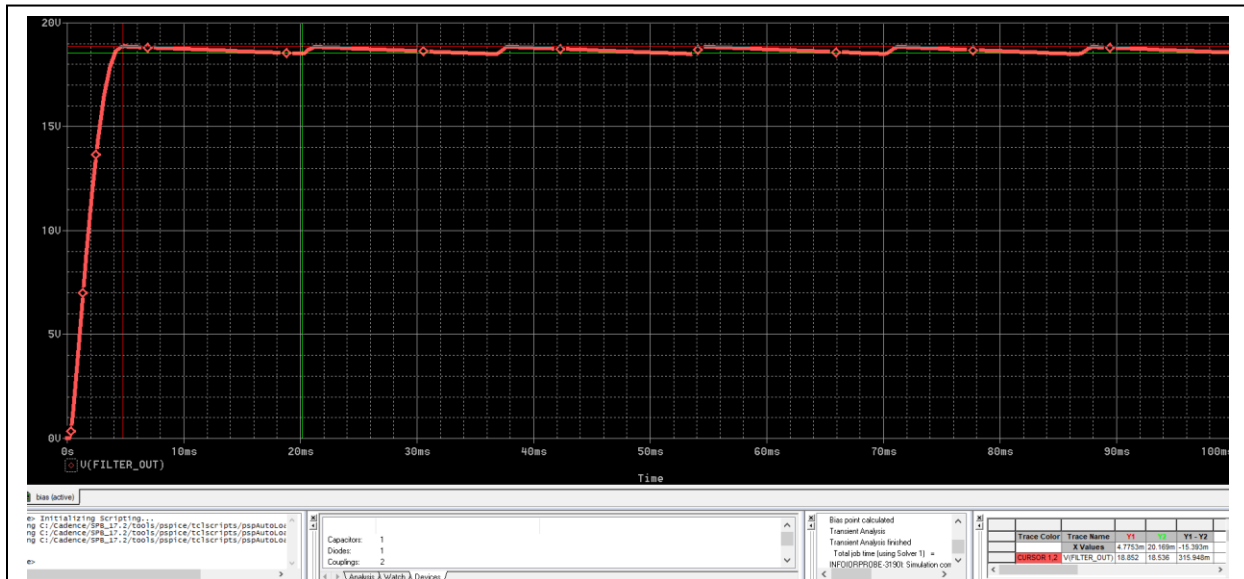

$$\text{Voltage Ripple} = 18.848 \text{ V} - 18.529 \text{ V} = .319 \text{ V}$$


DC power supply design 4(a)

Zener voltage = 5.1 V at 49 mA.

$$49 \text{ mA} = (18.848 \text{ V} - 5.1 \text{ V}) / R$$

$$\rightarrow R = 280.51 \text{ ohms}$$


DC power supply design 4(b)

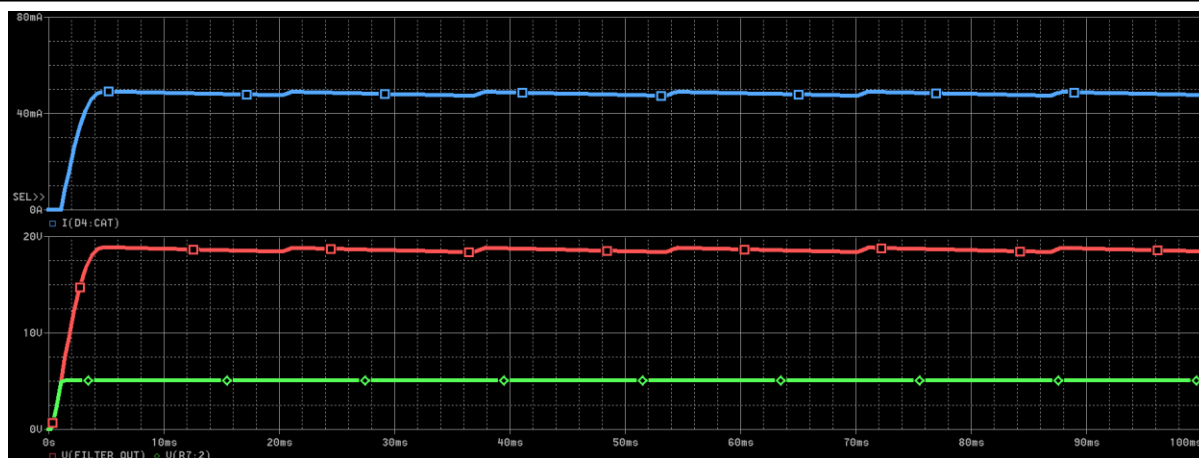

$$V(\text{REG_IN}) = .319 \text{ V} \quad V(\text{REG_OUT}) = 5.1002 \text{ V} - 5.0997 \text{ V} = .0005 \text{ V}$$

$$\text{Line Regulation} = .0005 \text{ V} / .319 \text{ V} = 1.57 \text{ mV/V}$$

DC power supply design 5(a)

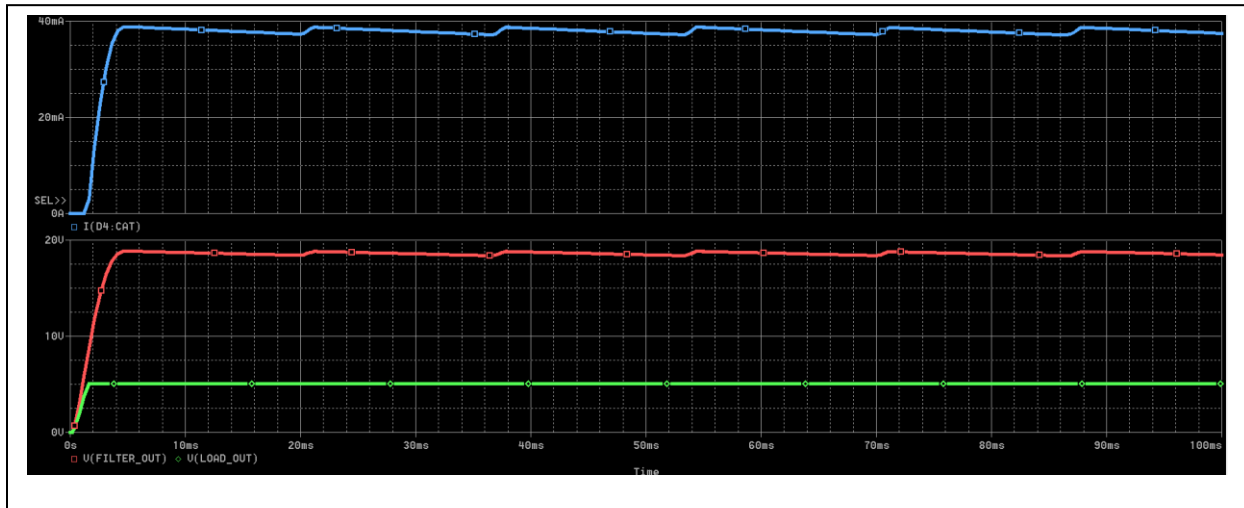

DC power supply design 5(b)

$$\text{Ripple 1} = 18.852 \text{ V} - 18.431 \text{ V} = .421 \text{ V}$$

$$\text{Ripple 2} = 5.0966 \text{ V} - 5.0960 \text{ V} = .0006 \text{ V}$$


$$\text{Line Regulation} = .0006 \text{ V} / .421 \text{ V} = 1.43 \text{ mV/V}$$

The ripple voltages increase for both measured values because the current through the Zener diode decreases, meaning it is not as far in the breakdown region.

DC power supply design 5(c)

I changed the capacitance in the filter circuit, which led to an improvement in the line regulation. Increasing the capacitance increases the time constant, which means that it will take longer for the voltage to decrease to a specified voltage. Likewise, when being measured at a specific point in time, the voltage will not be able to decrease as much, effectively decreasing the ripple voltage.

DC power supply design 5(d)

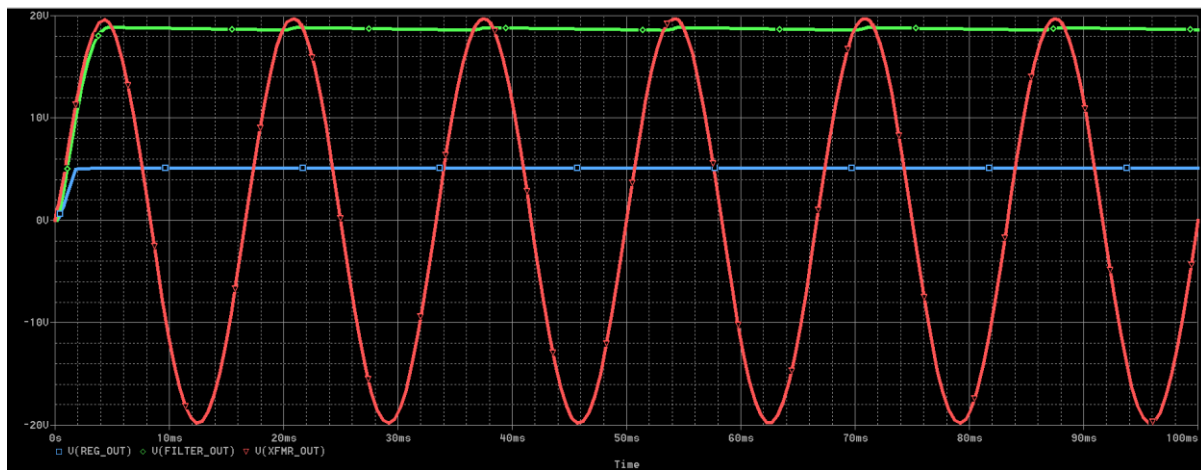

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]