

Extra Credit Assignment (Option #3)

ECE 0257 – Spring 2019

Name

Avery Peiffer

Hand Analysis

(a)

Simulation

(a)


Prototype

(a)-(g)


Check-list Before Submission

- ☐ Write within boxes, no boxes are moved
- ☐ Write your full names in designated area
- ☐ Save this file as a PDF before uploading, keep the number of pages (**13**) unchanged
- ☐ Notify “TO BE CONTINUED” accordingly if you used the extra pages (page 11-13)


Hand Analysis (a)

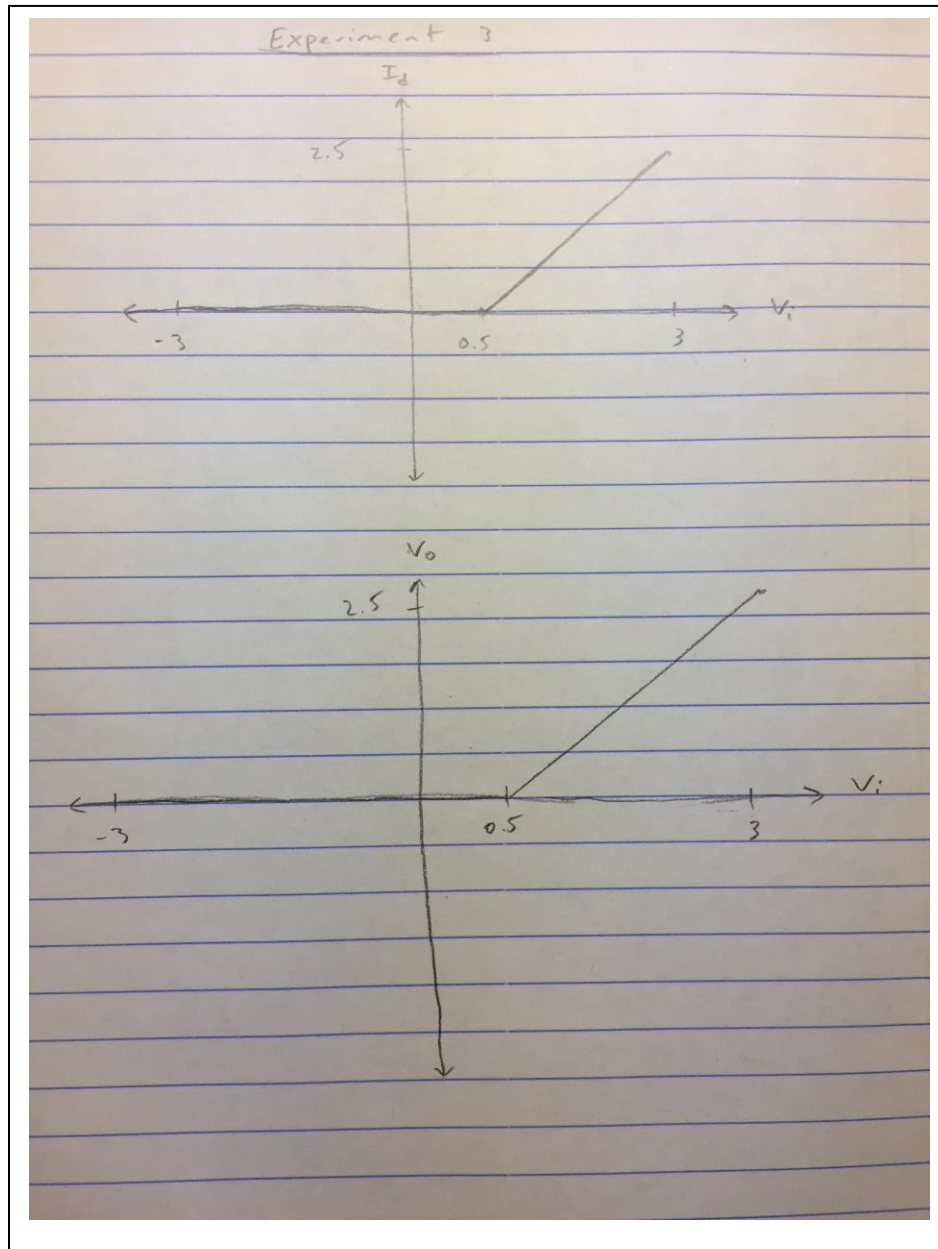

Simulation (a)

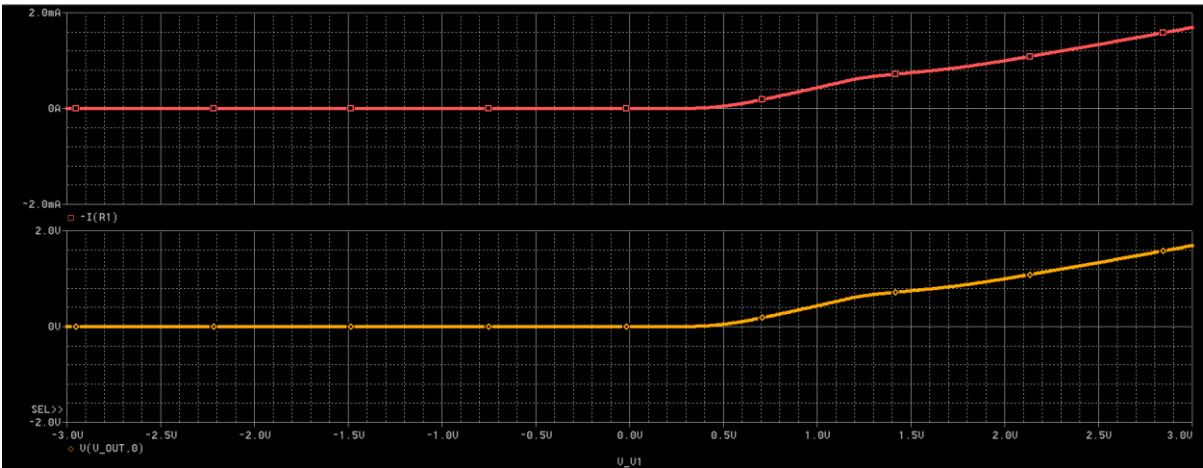

Prototype (a)

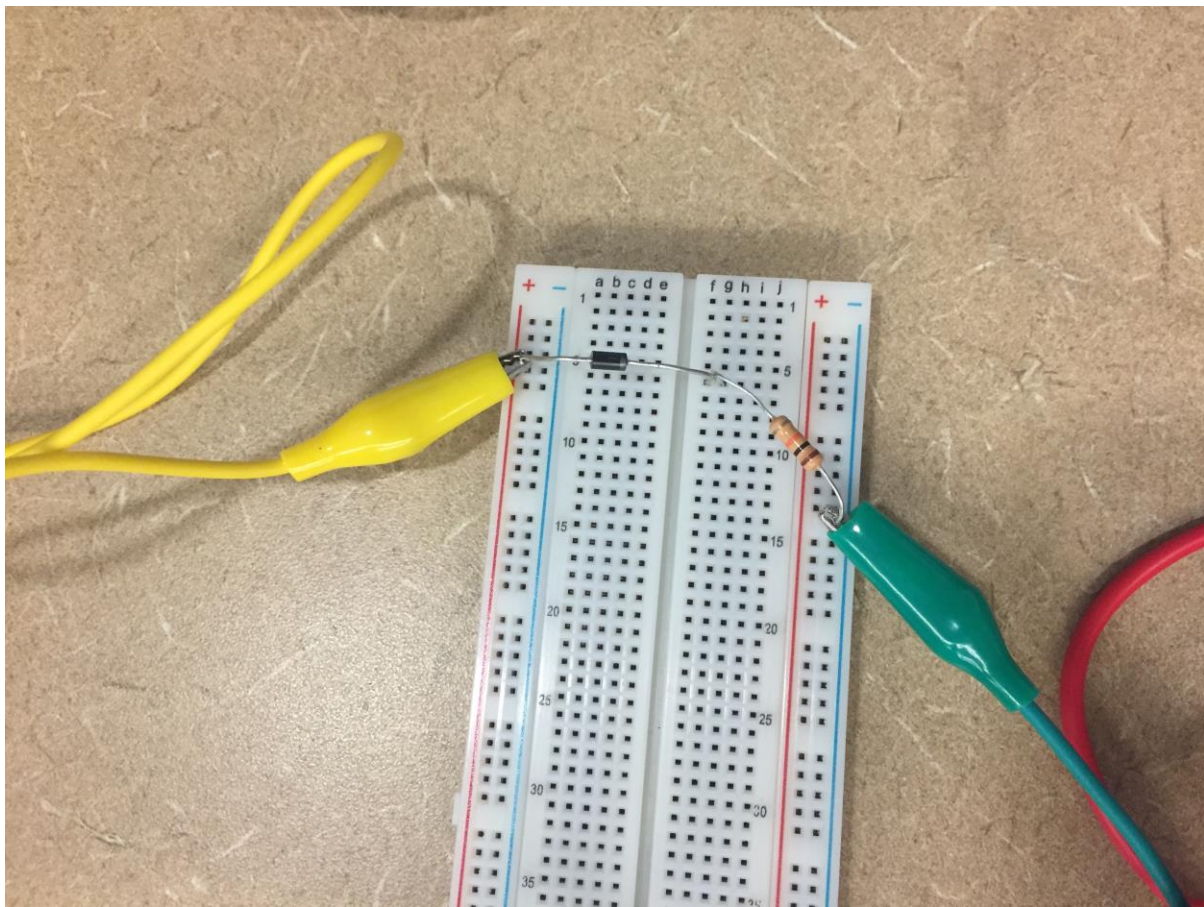


Prototype (b)

Resistance = 0.993 kilohms


Prototype (c)

Vi	Vo (V)	Id = Ir (mA)
-3	-0.000003	-0.000003
-2.75	-0.000005	-0.000005
-2.5	-0.0000025	-2.5E-06
-2.25	-0.000002	-0.000002
-2	-0.000002	-0.000002
-1.75	-0.000002	-0.000002
-1.5	-0.000001	-0.000001
-1.25	-0.000001	-0.000001
-1	-0.000001	-0.000001
-0.75	-0.000001	-0.000001
-0.5	-0.000001	-0.000001
-0.25	-0.000001	-0.000001
0	0	0
0.25	0.00022	0.00022
0.5	0.0465	0.0465
0.75	0.227	0.227
1	0.445	0.445
1.25	0.675	0.675
1.5	0.909	0.909
1.75	1.148	1.148
2	1.388	1.388
2.25	1.631	1.631
2.5	1.874	1.874
2.75	2.118	2.118
3	2.363	2.363


Prototype (d)

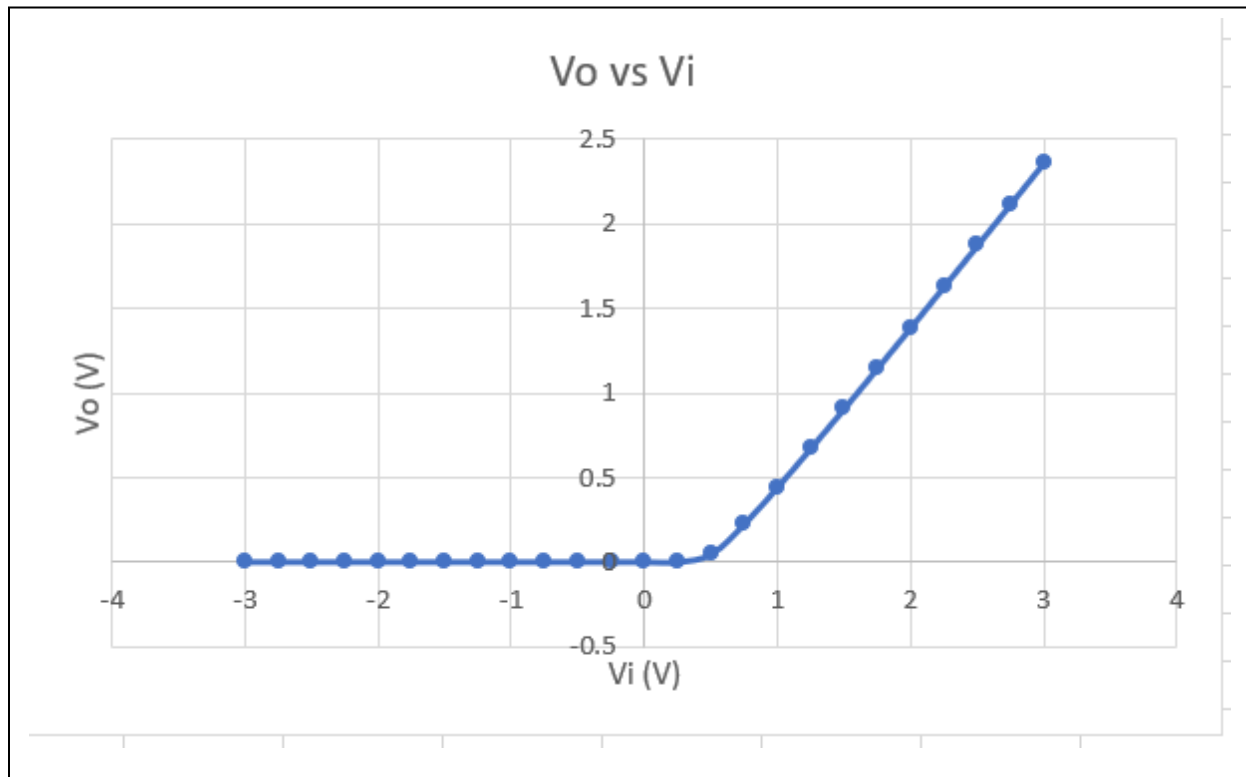

Prototype (e)

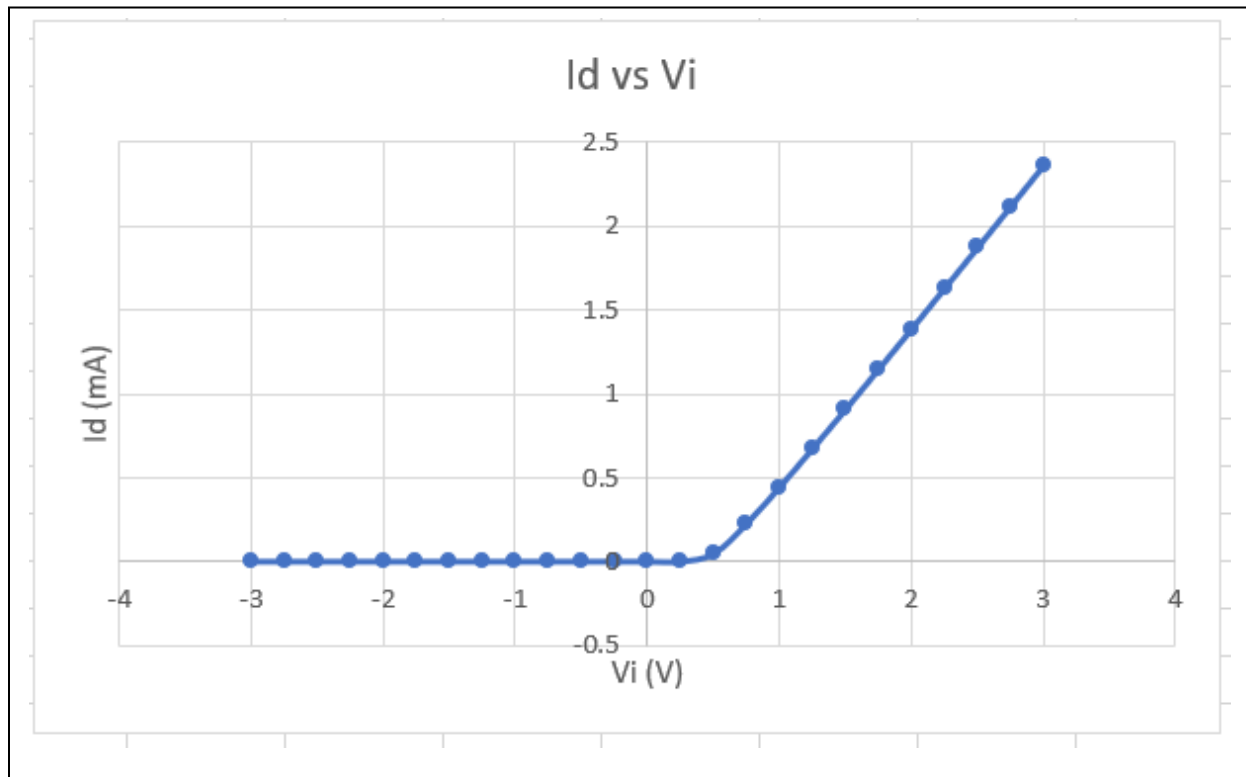

Prototype (f)

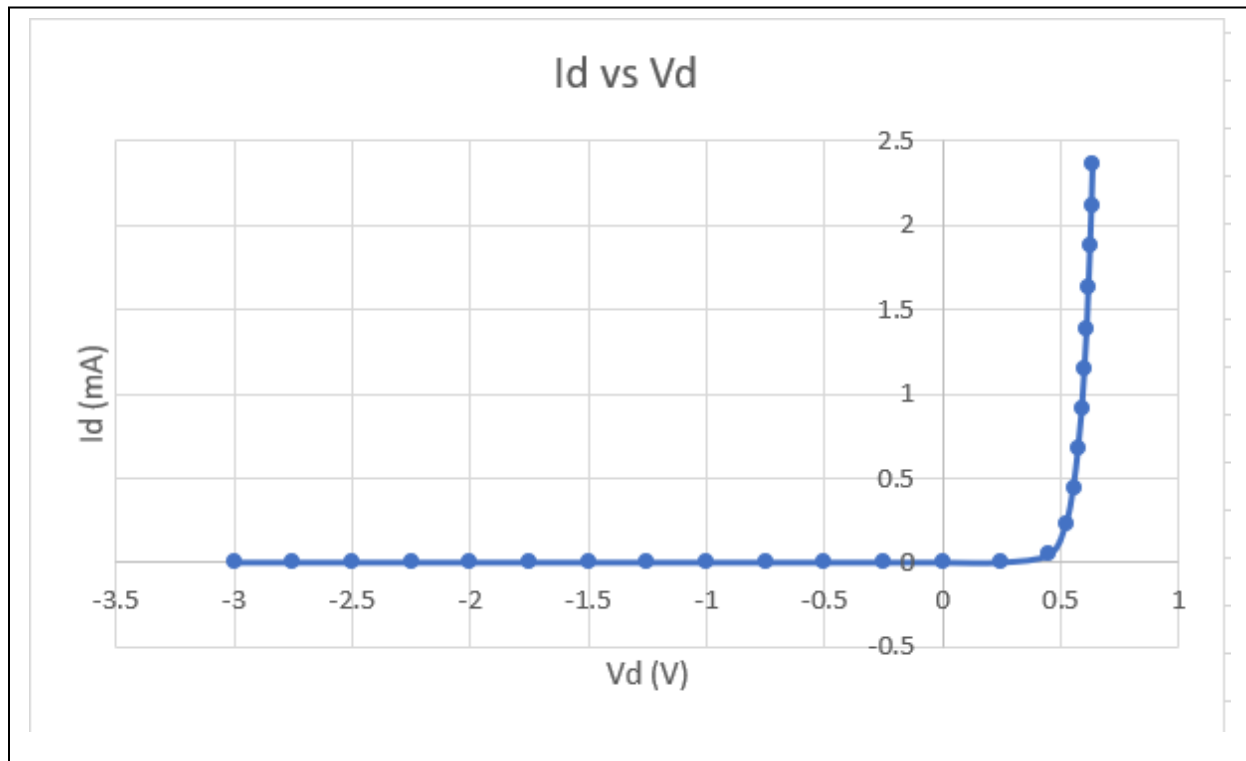

Prototype (g)

There is a slight discrepancy between the hand calculations/measurements and the simulation. In the simulation, the curve is not entirely linear from 0.5 V – 1.5 V. I attribute this to the PSpice model of a diode being more detailed than the precision used for the hand calculations and measurements. This distortion in the curves is likely due to the diode being a non-linear device and not entirely fitting the model used for it throughout the experiment.

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]